

Get an ADSR waveform from a few components


An SN 7401N TTL quad gate, three transistors and a few discrete components constitute an attack-delay-sustain-release (ADSR) waveform generator of the type used in electronic music synthesizers. The four waveform "variables" are independently adjustable over a wide range, with a maximum output amplitude of 8 V. The circuit also doubles as a simple attack-release generator for simulating percussion voicing.

A positive-going TTL input is needed to operate the circuit (Fig. 1). After being inverted (gate 4) and differentiated (2.2 k Ω , 470 pF RC network). The input signal turns on the RS flip-flop (gates 1 and 2). Capacitor C is charged via P₃, D₁, P₁, and R₁, to produce the attack time. The length of the attack time, t₁, is determined by P₁ (Fig. 2).

When the voltage across C reaches 8 V, Q₁ opens and switches off the flip-flop, initiating the decay period t₂. The length of t₂ is determined by P₂.

At a voltage level determined by P₃, D₂ conducts and C stops discharging, initiating the sustain level. This level is maintained until the TTL input signal goes low.

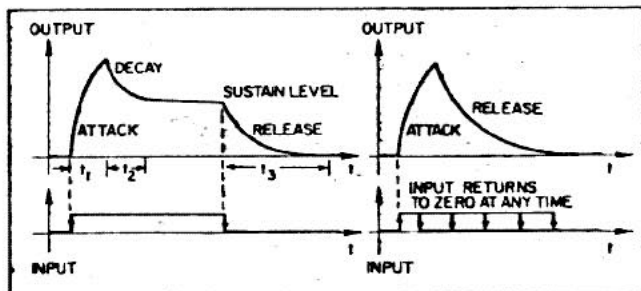When the TTL input goes low, gate 3's output goes low too. Gate 3 continues the discharging of C via




2. The circuit operates in two modes: attack-delay-sustain-release (left) or attack-release (right). The duration of the TTL input signal is significant only in the ADSR mode.

P₄. Release time t₃ is created and its duration is determined by P₄.

When used simply as an attack-release generator (by setting the operating mode switch in position 2), the circuit produces a waveform "envelope" suitable for percussion voicing. In this mode, the release time begins directly after the attack time, regardless of when the positive TTL input signal returns to zero.

Örley Gábor, Electrical Engineer, 1111. Budapest, XI., Egri Jozsef u.36., Hungary.

CIRCLE 311

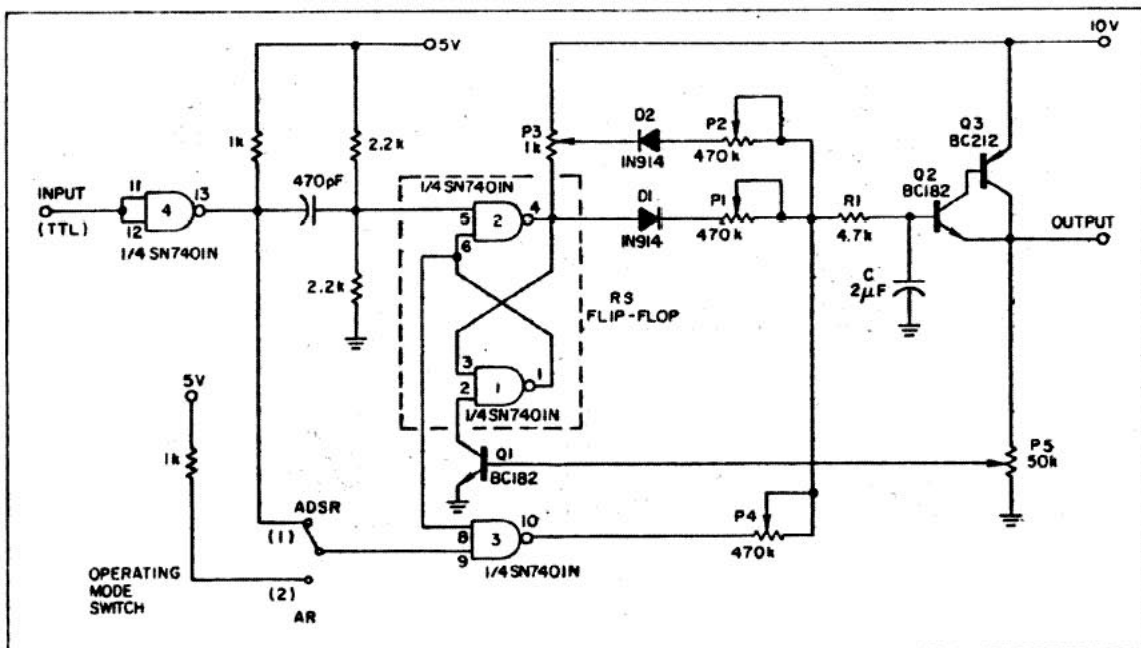

1. The "attack," "decay," and "release" intervals of this ADSR waveform generator are independently adjustable using P₁, P₂, and P₃, respectively. The "sustain" interval is determined by the positive period of the input signal.