

Voltage-controlled integrator sets filter's bandwidth

by Henrique Sarmento Malvar
Department of Electrical Engineering, University of Brasilia, Brazil

Because it uses operational transconductance amplifiers as electrically tuned integrators for selecting a state-variable filter's center frequency and bandwidth virtually independently of one another, this circuit is ideal for use in music and speech synthesizers that require individual voltage-controlled setting of these parameters.

As shown, input signals to be processed are applied to transconductance amplifier A_1 , whose bias current is derived from voltage-to-current driver $A_5 Q_5$. The bias current, in turn, is set by control voltage V_ω , which ultimately determines the filter's center frequency. In general, $I_{bias} = V_\omega / 2R_{11}$.

Placing the capacitor C_ω across the output of the operational transconductance amplifiers A_1 and A_2 converts the two-stage network into a noninverting integra-

tor, the transfer function becoming $V_o(s)/V_i(s) = k/s$, where k is the 3080's transconductance factor k'/C , and transconductance k' as given in its data sheets is $k' = 19.2 I_{bias}$. Substituting for I_{bias} , $V_o(s)/V_i(s) = 19.2 V_\omega / sRC\omega$.

Placing integrator A_3 in the feedback loop of A_1 and A_2 equips the basic filter with the capability to control bandwidth. As seen from inspection of the circuit:

$$V_x(s) = R_1 |R_2| R_3 |R_4 \left[\frac{V_1(s)}{R_1} + \frac{V_y(s)}{R_3} + \frac{V_{LP}(s)}{R_4} \right]$$

where the low-pass function is given by:

$$V_{LP}(s) = -(k_2/s)^2 V_x(s) R_6 / (R_5 + R_6)$$

and where $V_y(s) = -k_1 V_x(s)/s$. Constants k_1 and k_2 are given by:


$$k_1 = 19.2 V_B / R_7 C_B$$

$$k_2 = 19.2 V_\omega / 2R_{11} C_\omega$$

and the bandpass function, $V_{BP}(s)$, equals $-k_2 V_x(s)/s$.

Assuming $R_1 = R_3 = R_4 = R_5 = R'$ and $R_2 = R_6 = R''$, with $R''/R' = a \ll 1$, it follows that $R_1 |R_2| R_3 |R_4 = R_2$. Substituting the appropriate quantities back into all the above equations, it is seen that:
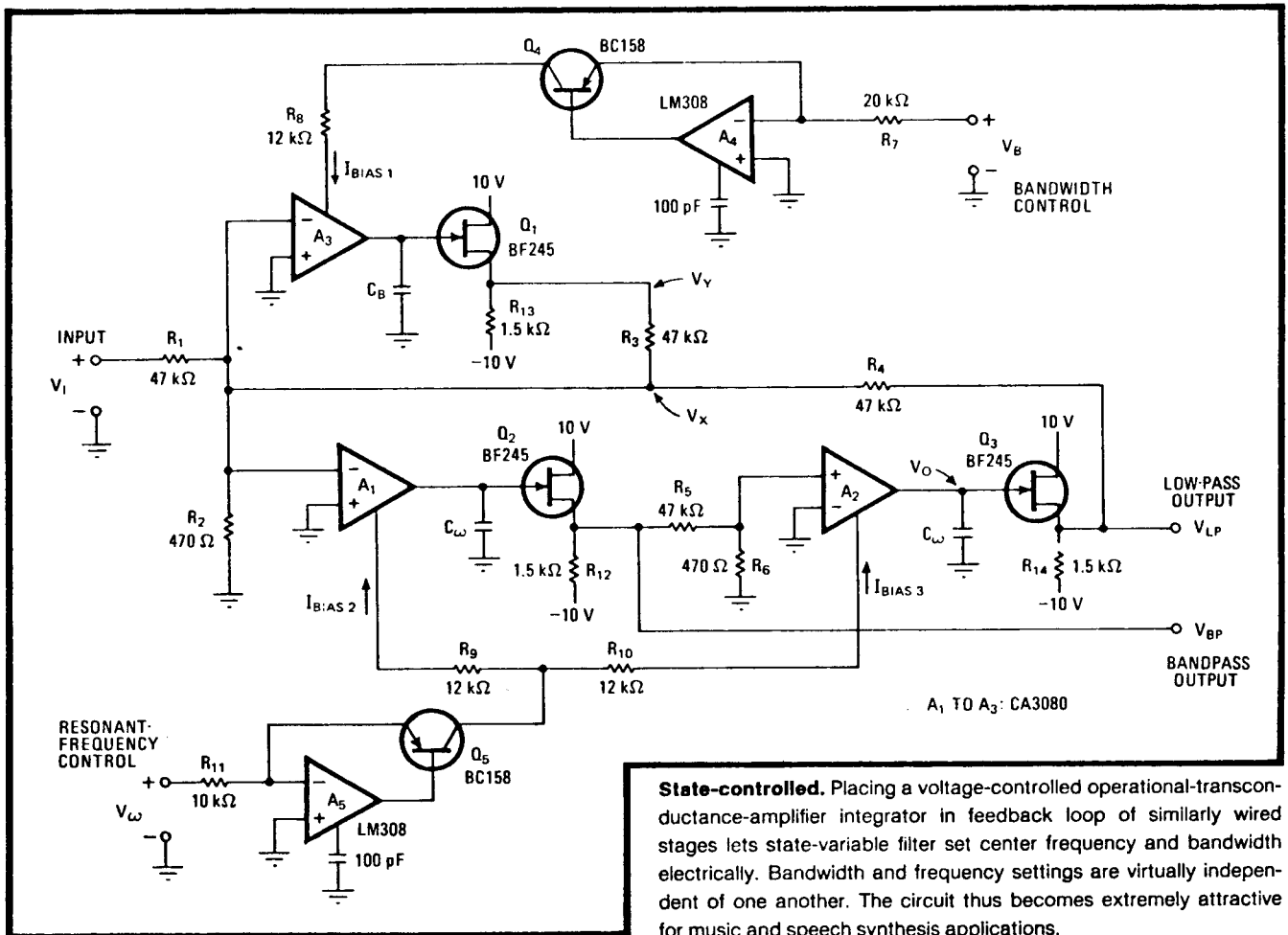
$$V_{LP}(s)/V_i(s) = -1 / [(s/\omega_0)^2 + (B/\omega_0)(s/\omega_0) + 1]$$



State-controlled. Placing a voltage-controlled operational-transconductance-amplifier integrator in feedback loop of similarly wired stages lets state-variable filter set center frequency and bandwidth electrically. Bandwidth and frequency settings are virtually independent of one another. The circuit thus becomes extremely attractive for music and speech synthesis applications.

$$V_{BP}(s)/V_i(s) = -(s/\omega_0) / [(s/\omega_0)^2 + (B/\omega_0)(s/\omega_0) + 1]$$

Where the resonant frequency and the bandwidth are given by: ω_0 (rad/s) = $a k_2 = 19.2 a V_\omega / 2R_{11} C_\omega$

$$B$$
 (rad/s) = $a k_1 = 19.2 a V_B / R_7 C_B$

Parameter a should be near 0,01 to ensure the best compromise